

Chapter 2 :: Combinational Logic Design

(조합 논리 설계)

Digital Design and Computer Architecture

David Money Harris and Sarah L. Harris

Lectured by Jeong-Gun Lee @ Hallym



Chapter 2 :: Topics

- **Introduction** (소개)
- **Boolean Equations** (부울 식, 이진논리식)
- **Boolean Algebra** (부울대수)
- **From Logic to Gates** (논리에서 회로로...)
- **Multilevel Combinational Logic** (다층 조합회로)
- **X's and Z's, Oh My** (X와 Z?)
- **Karnaugh Maps** (카르노 맵)
- **Combinational Building Blocks** (조합회로 블록)
- **Timing** (타이밍)




Introduction

A logic circuit is composed of:


(논리 회로는 다음 등으로 이루어진다)

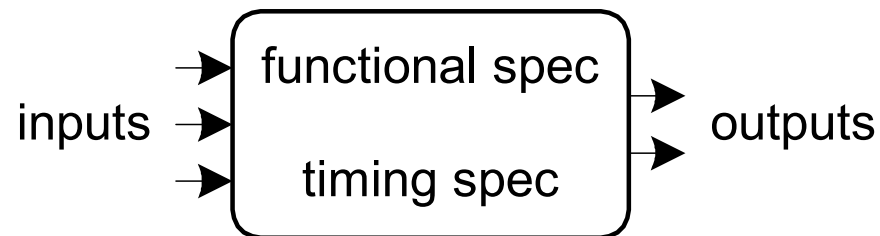- Inputs (입력)
- Outputs (출력)
- Functional specification (기능)
- Timing specification (타이밍)




Circuits (회로)

 - Nodes (노드)
 - Inputs: A, B, C
 - Outputs: Y, Z
 - Internal: $n1$
- Circuit elements (회로 구성요소)
 - $E1, E2, E3$
 - Each a circuit




Types of Logic Circuits

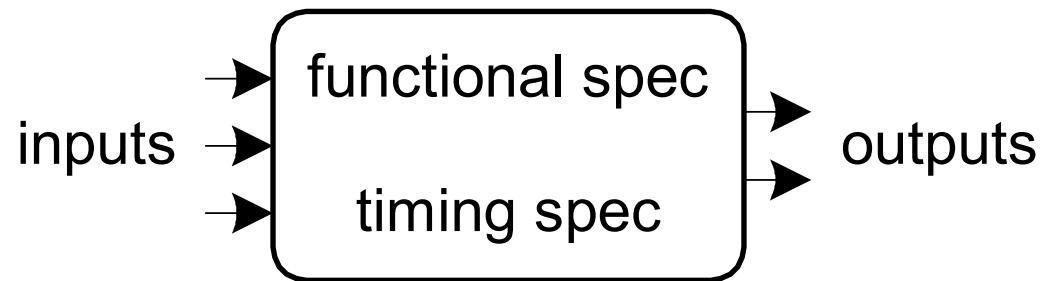- Combinational Logic (조합회로)
 - Memoryless (메모리 없음)
 - Outputs determined by current values of inputs
(출력이 현재의 입력 값에 의해 결정됨)
- Sequential Logic (조합회로)
 - Has memory (메모리 가짐)
 - Outputs determined by previous and current values of inputs
(출력이 현재와 이전 입력에 의존하여 결정됨)



Rules of Combinational Composition

 - Every circuit element is itself combinational
- Every node of the circuit is either designated as an input to the circuit or connects to exactly one output terminal of a circuit element
- The circuit contains *no cyclic paths*: every path through the circuit visits each circuit node at most once
- Example:




Boolean Equations (부울식)

- Functional specification of outputs in terms of inputs
- Example:

$$S = \mathbf{F}(A, B, C_{\text{in}})$$
 
$$C_{\text{out}} = \mathbf{F}(A, B, C_{\text{in}})$$



$$S = A \oplus B \oplus C_{\text{in}}$$
$$C_{\text{out}} = AB + AC_{\text{in}} + BC_{\text{in}}$$



Sum-of-Products (SOP) Form

- All Boolean equations can be written in SOP form
- Each row in a truth table has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- The function is formed by ORing the minterms for which the output is **TRUE**
- Thus, a sum (OR) of products (AND terms)

A	B	Y	minterm
0	0	0	$\overline{A} \overline{B}$
0	1	1	$\overline{A} B$
1	0	0	$A \overline{B}$
1	1	1	$A B$

$$Y = F(A, B, C) = \overline{A}B + AB$$



Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row in a truth table has a **maxterm**
- A maxterm is a sum (OR) of literals
- Each maxterm is FALSE for that row (and only that row)
- The function is formed by *ANDing the maxterms* for which the output is **FALSE**
- Thus, a product (AND) of sums (OR terms)

A	B	Y	maxterm
0	0	0	$A + B$
0	1	1	$A + \overline{B}$
1	0	0	$\overline{A} + B$
1	1	1	$\overline{A} + \overline{B}$

$$Y = F(A, B, C) = (A + B)(\overline{A} + B)$$



SOP = POS ?

$$\begin{aligned} Y = F(A, B, C) &= \overline{A}B + AB \\ &= (\overline{A} + A)B = 1B = \mathbf{B} \\ &= (1 + A + \overline{A})B = B + AB + \overline{A}B \end{aligned}$$

$$\begin{aligned} Y = F(A, B, C) &= (A + B)(\overline{A} + B) \\ &= A\overline{A} + AB + \overline{A}B + BB \\ &= AB + \overline{A}B + B \\ &= (A + \overline{A} + 1)B = 1B = \mathbf{B} \end{aligned}$$



Boolean Equations Example

- You are going to the cafeteria for lunch
 - You won't eat lunch (\bar{E})
 - If it's not open (\bar{O}) or
 - If they only serve corndogs (C)
- Write a truth table for determining if you will eat lunch (E).



O	C	E
0	0	0
0	1	0
1	0	1
1	1	0

SOP & POS Form

- SOP – sum-of-products

O	C	E	minterm
0	0	0	$\overline{A} \overline{B}$
0	1	0	$\overline{A} B$
1	0	1	$A \overline{B}$
1	1	0	$A B$

$$Y = A\overline{B}$$

- POS – product-of-sums

O	C	E	maxterm
0	0	0	$A + B$
0	1	0	$A + \overline{B}$
1	0	1	$\overline{A} + B$
1	1	0	$\overline{A} + \overline{B}$

$$Y = (A + B)(A + \overline{B})(\overline{A} + \overline{B})$$



Boolean Algebra

- Set of axioms and theorems to **simplify Boolean equations**
- Like regular algebra, but in some cases simpler because variables can have only two values (1 or 0)
- Axioms and theorems obey the **principles of duality**:
 - ANDs and ORs interchanged, 0's and 1's interchanged



Boolean Axioms and Theorems



Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

Theorem		Dual		Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements





T1: Identity Theorem

- $B \bullet 1 = B$
- $B + 0 = B$

  



T2: Null Element Theorem

- $B \bullet 0 = 0$
- $B + 1 = 1$

  


T3: Idempotency Theorem

- $B \bullet B = B$
- $B + B = B$

  



T4: Identity Theorem

- $\overline{\overline{B}} = B$

 

T5: Complement Theorem

  - $B \cdot \overline{B} = 0$
- $B + \overline{B} = 1$



Boolean Theorems of Several Variables

Theorem		Dual		Name
T6	$B \bullet C = C \bullet B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \bullet C) + B \bullet D = B \bullet (C + D)$	T8'	$(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	T9'	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	T10'	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D)$ $= B \bullet C + \overline{B} \bullet D$	T11'	$(B + C) \bullet (\overline{B} + D) \bullet (C + D)$ $= (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots}$ $= (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots}$ $= (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots)$	De Morgan's Theorem



Simplifying Boolean Expressions: Example 1

- $$\begin{aligned} Y &= \overline{A}B + AB \\ &= B(\overline{A} + A) && \text{T8} \\ &= B(1) && \text{T5'} \\ &= B && \text{T1} \end{aligned}$$



Simplifying Boolean Expressions: Example 2

- $Y = B(AB + ABC)$

$$= A(AB(1 + C)) \quad \text{T8}$$

$$= A(AB(1)) \quad \text{T2'}$$

$$= A(AB) \quad \text{T1}$$



$$= (AA)B \quad \text{T7}$$

$$= AB \quad \text{T3}$$





DeMorgan's Theorem

  - $Y = \overline{AB} = \overline{A} + \overline{B}$



  - $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$



Bubble Pushing

- Pushing bubbles backward (from the output) or forward (from the inputs) changes the body of the gate from AND to OR or vice versa.
- Pushing a bubble from the output back to the inputs puts bubbles on all gate inputs.




- Pushing bubbles on *all* gate inputs forward toward the output puts a bubble on the output and changes the gate body.




Bubble Pushing

 - What is the Boolean expression for this circuit?



Bubble Pushing

 
- What is the Boolean expression for this circuit?






$$Y = AB + CD$$

Bubble Pushing Rules

 - Begin at the output of the circuit and work toward the inputs.
- Push any bubbles on the final output back toward the inputs.
- Working backward, draw each gate in a form so that bubbles cancel.



Bubble Pushing Rules

   


$$Y = \overline{A}\overline{B}C + \overline{D}$$



From Logic to Gates

 - Two-level logic: ANDs followed by Ors
- Example: $Y = \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + A\overline{B}C$



Circuit Schematic Rules

(회로 그림 규칙)


- Inputs are on the left (or top) side of a schematic
입력은 왼쪽 또는 위쪽에...
- Outputs are on the right (or bottom) side of a schematic
출력은 오른쪽 또는 아래쪽에...
- Whenever possible, gates should flow from left to right
가능한 회로는 왼쪽에서 오른쪽으로 데이터가 흐르게...
- Straight wires are better to use than wires with multiple corners
가능하면 선은 일직선으로...




Circuit Schematic Rules (cont.)

- Wires always connect (연결) at a T junction
- A dot where wires cross indicates a connection between the wires
- Wires crossing *without* a dot make no connection


wires connect
at a T junction

 


wires connect
at a dot

 

 wires crossing
without a dot do
not connect



Multiple Output Circuits

 


A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0



Priority Encoder Hardware

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

 

Don't Cares


A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0



Contention: X

 
- Contention: circuit tries to drive the output to 1 and 0



Floating: Z

- Floating, high impedance, open, high Z
- Output is not connected to the input

Tristate Buffer

 

E	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1



Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
- K-maps minimize equations graphically
- $PA + P\bar{A} = P$

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Y C		AB			
		00	01	11	10
0		1	0	0	0
1		1	0	0	0

Y C		AB			
		00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$



K-map

- Circle 1's in adjacent squares
- In the Boolean expression, include only the literals whose true and complement form are *not* in the circle

		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	0	0	0

$$Y = \overline{A}\overline{B}$$



K-map Example

Y C \ AB		00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

Truth Table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

K-Map

Y C \ AB		00	01	11	10
0		0	1	0	0
1		0	1	0	1

$$Y = \bar{A}B + A\bar{B}C$$



3-input K-map

		AB			
		00	01	11	10
C	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

Truth Table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

K-Map

		AB			
		00	01	11	10
C	0	0	1	1	0
	1	0	1	0	0

$$Y = \bar{A}B + B\bar{C}$$



K-map Definitions

- Complement: variable with a bar over it
 $\bar{A}, \bar{B}, \bar{C}$
- Literal: variable or its complement
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- Implicant: product of literals
 $AB\bar{C}, \bar{A}C, BC$
- Prime implicant: implicant corresponding to the **largest circle** in a K-map



K-map Rules

- **Each circle must span a power of 2** (i.e. 1, 2, 4) squares in each direction
- Each circle must be **as large as possible**
- A circle may **wrap around the edges** of the K-map
- A one in a K-map may be **circled multiple times**
- A “don't care” (X) is circled only if it helps minimize the equation



4-input K-map

Y		AB			
CD		00	01	11	10
	00	1	0	0	1
01	01	0	1	0	1
	11	1	1	0	0
10	10	1	1	0	1

$$Y = \bar{A}\bar{C} + \bar{A}BD + A\bar{B}\bar{C} + \bar{B}\bar{D}$$



K-Maps with Don't Cares

Y CD \ AB		AB			
		00	01	11	10
00	1	0	X	1	
01	0	X	X	1	
11	1	1	X	X	
10	1	1	X	X	

$$Y = A + \overline{B}\overline{D} + C$$




Combinational Building Blocks

- Multiplexers (멀티플렉서)
- Decoders (디코더)



Multiplexer (Mux:멀스)

 - Selects between **one of N inputs** to connect to the output.
- $\log_2 N$ -bit select input – control input
- Example: 2:1 Mux




S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		

Logic using Multiplexers

- Using the mux as a lookup table – AND-gate
(멀스를 참조테이블로 사용하여 논리게이트 만들기)

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = AB$$

 


Logic using Multiplexers

- Reducing the size of the mux (믹스의 사이즈 줄이기)

$$Y = AB$$


<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	0
1	0	0
1	1	1

<i>A</i>	<i>Y</i>
0	0
1	<i>B</i>

 

Decoders

 
- N inputs, 2^N outputs
- **One-hot outputs:** only one output HIGH at once
출력 신호들 중 단 하나의 값만 '1'을 갖는다.



A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0


Logic using Decoders (디코더를 이용한 회로)

- OR minterms

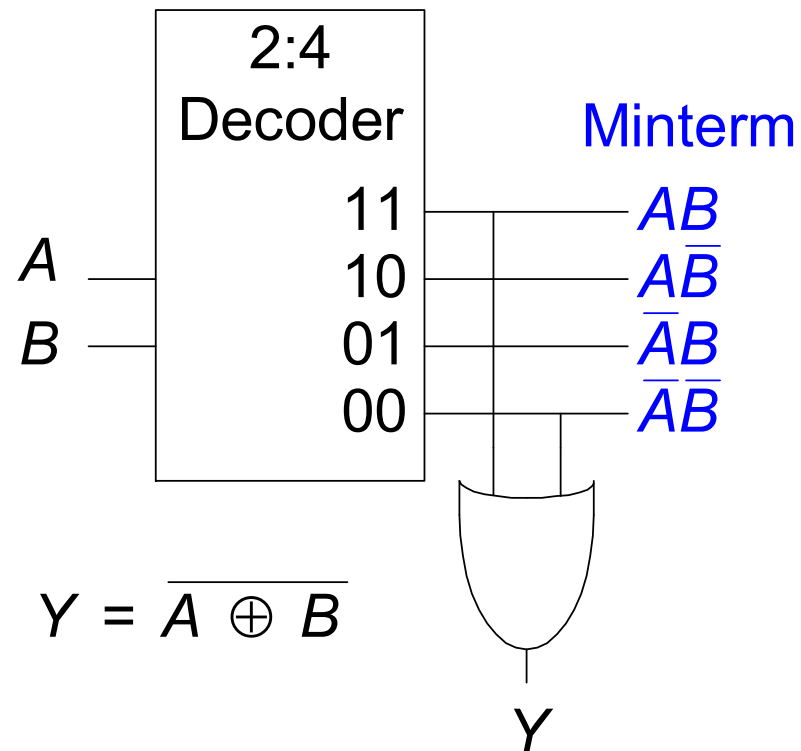


Timing (타이밍)

 - **Delay between input change and output changing**
- One of the biggest challenges in circuit design: **making the circuit fast**



Propagation & Contamination Delay (전파 및 혼합 지연)

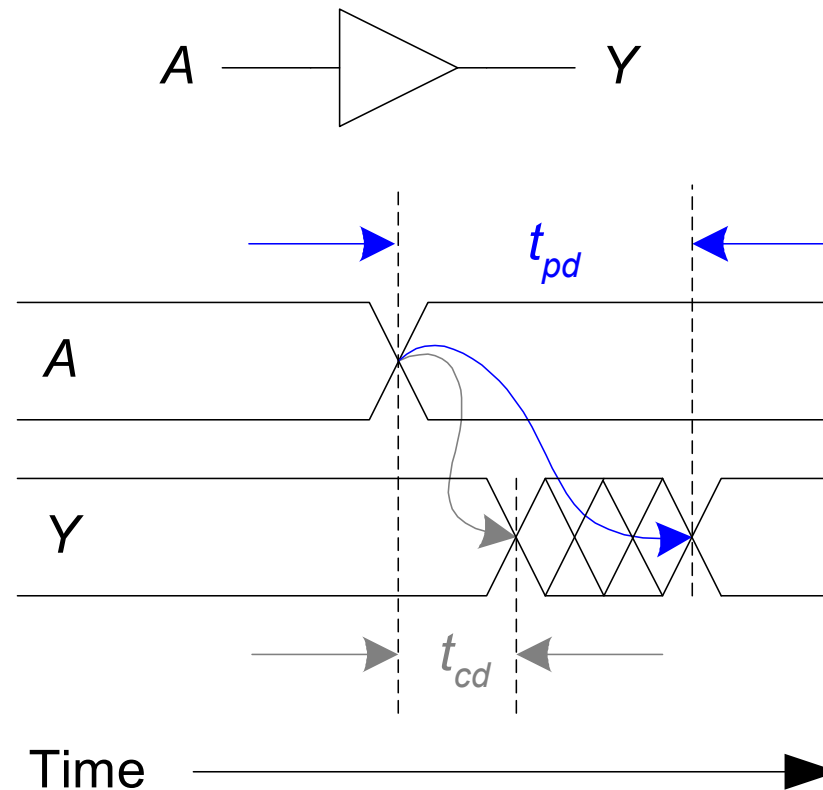- Propagation delay: t_{pd} = max delay from input to output
- Contamination delay: t_{cd} = min delay from input to output




Propagation & Contamination Delay

- Delay is caused by
 - Capacitance and resistance in a circuit
 - Speed of light limitation
- Reasons why tpd and tcd may be different:
 - Different rising and falling delays
상승지연과 하강지연이 다르다.
 - Multiple inputs and outputs, some of which are faster than others
입력이나 출력이 여러 개 있을 경우, 서로간의 속도 차가 있다.
 - Circuits slow down when hot and speed up when cold
회로는 뜨거울 때 속도가 느리고, 차가울 때 속도가 빨라진다.



Critical and Short Paths (임계 경로 및 짧은 경로)

 

Critical (Long) Path: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$


Short Path: $t_{cd} = t_{cd_AND}$

Glitches (글리치)

- A glitch occurs when a single input change causes multiple output changes
(단일 입력의 변화가 다수의 출력의 유도할 때)
- Glitches don't cause problems because of synchronous design conventions (which we'll talk about in Chapter 3)
(동기식 회로에서는 문제를 야기하지 않음)
- But it's important to recognize a glitch when you see one in simulations or on an oscilloscope
(하지만 존재에 대해서 이해하고 해석할 능력은 필요함)



Glitch Example


 


		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC$$



Glitch Example (cont.)

  


Glitch Example (cont.)

		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$\bar{A}\bar{C}$

$$Y = \bar{A}\bar{B} + BC + \bar{A}C$$

 

Why Understand Glitches?

- Recognize them when look at timing diagrams in (simulations or on an oscilloscope)
- Can't get rid of all glitches – simultaneous transitions on multiple inputs can also cause glitches

